



NFC Reader Design: Antenna design considerations

Public

MobileKnowledge
February 2015

Agenda

- ▶ Introduction to RFID and NFC
- ▶ Contactless reader design:
 - Initial considerations and architecture
- ▶ Illustrative contactless reader schematics:
 - RFID Elektor schematic
 - CLRC663 Point of Sales schematic
- ▶ NXP portfolio
 - NFC Reader IC overview
 - LPC microcontrollers overview

Previous session

- ▶ NFC Reader Antenna design
 - Antenna principles
 - Antenna matching steps
 - Environmental influences
 - Testing & antenna qualification


For an in depth-training,
please refer to the webinar series on
antenna design of Renke Bienert
www.nxp.com/products/related/customer-training.html



Recap of the previous session

Steps to design a contactless reader

Typical contactless reader architecture

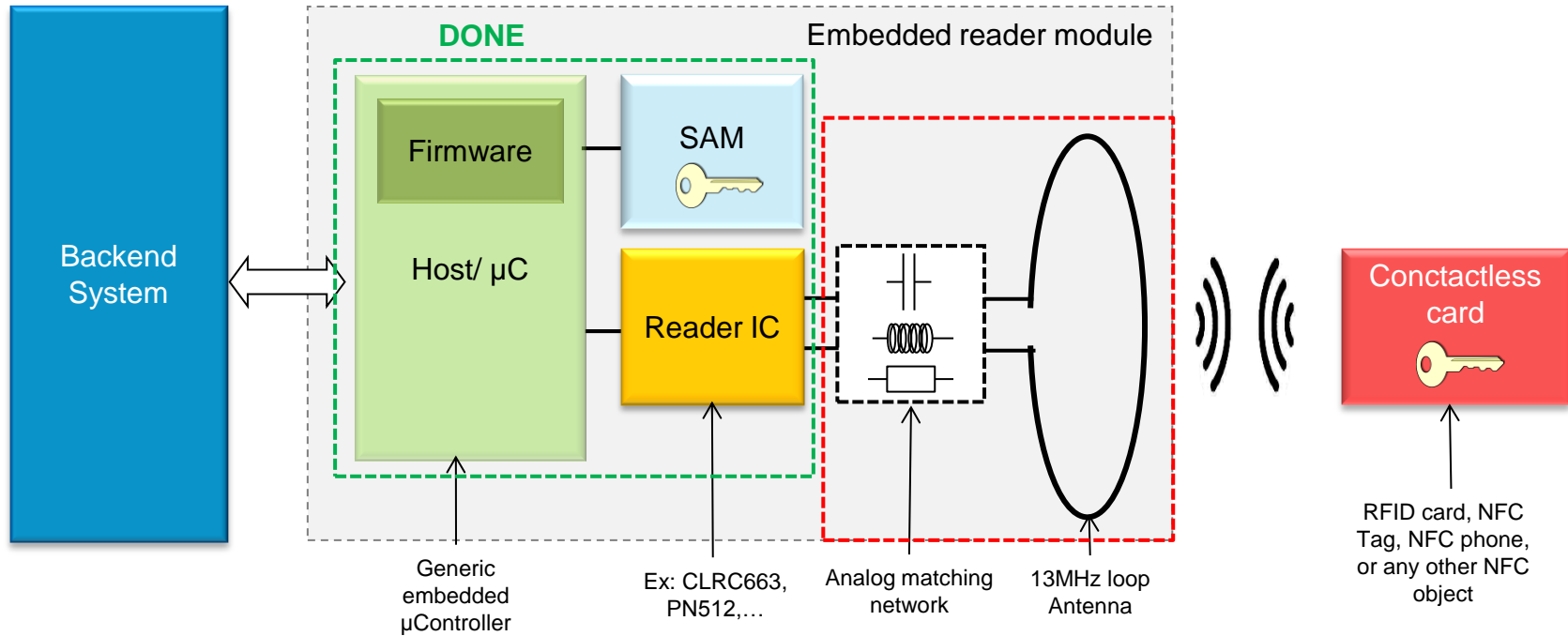

Steps to design a contactless reader

1

Selection of **contactless reader IC**

Which transponder do we need to interact with?

- ▶ Support of various RF standards
 - Dedicated use case & application may support only ISO/IEC 14443-A
 - Open application needs to support various RF standards such as ISO/IEC14443 A&B, ISO/IEC 15693
- ▶ Application specific requirements
 - EMVCo -> payments
 - NFC Forum -> Full NFC support on P2P and R&W
- ▶ Power consumption
 - Handheld contactless reader will require low energy consumption
- ▶ Selection of the host interface
 - SPI, I²C, RS232, UART ..
- ▶ Specific features
 - Specific data rates, timing and reading distance

Steps to design a contactless reader

1

Selection of **contactless reader IC**

Which transponder do we need to interact with?

2

Selection of **Host**

The brain and heart of our contactless reader

- ▶ External interfaces
 - Serial, USB, Ethernet
 - RF connectivity (BL, Wifi, Zigbee,...)
- ▶ SW architecture
 - How heavy or light are the processing power requirements? (MCU clock)
- ▶ Host architecture
 - Impact on development environment and source code libraries
- ▶ Memory requirements
 - Flash, RAM, ROM
- ▶ Power requirements
- ▶ Specific requirements
 - Secure EEPROM to store keys?
 - Crypto accelerators?
- ▶ Manufacturer support

Steps to design a contactless reader

1

Selection of **contactless reader IC**

Which transponder do we need to interact with?

2

Selection of **Host**

The brain and heart of our contactless reader

3

Selection of **security** architecture

SAM or Host for key storage

► Host / MCU

- Microcontrollers are not designed and developed to securely store and maintain cryptographic keys since they don't offer reliable protection and security mechanisms
- They do not widely implement HW-based crypto-processors, so the execution of these crypto algorithms is not efficient

► SAM

- It is a tamper-resistant chip that provides secure execution and secure key storage functions to the reader side
- It carries HW based cryptography that allows one to perform complex cryptographic operations efficiently
- **SAM X-interface:** It supports the X-mode, which allows a fast and convenient contactless terminal development by connecting the SAM to the microcontroller and reader IC simultaneously.

Steps to design a contactless reader

1

Selection of **contactless reader IC**
Which transponder do we need to interact with?

2

Selection of **Host**
The brain and heart of our contactless reader

3

Selection of **security** architecture
SAM or Host for key storage

4

Antenna design

Today's
session



5

GO!


Antenna principles

Magnetic field

- ▶ Magnetism is a phenomenon associated with the motion of electric charges. This motion can take many forms:
 - Charged particles moving through space
 - An electric current in a conductor
- ▶ The direction of such a magnetic field can be determined by using the “right hand grip rule”
 - Magnetic field lines form in concentric circles around a cylindrical current-carrying conductor such as a wire.
- ▶ Conductor loops are used as magnetic antennas to generate a magnetic alternating field in reader devices
- ▶ The strength of the magnetic field decreases with the distance from the wire.

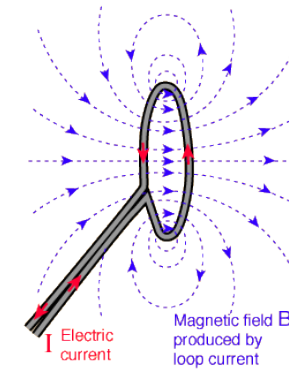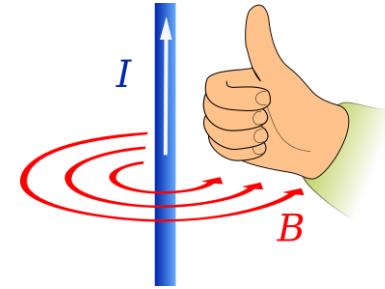


NFC antenna: Transformer principle

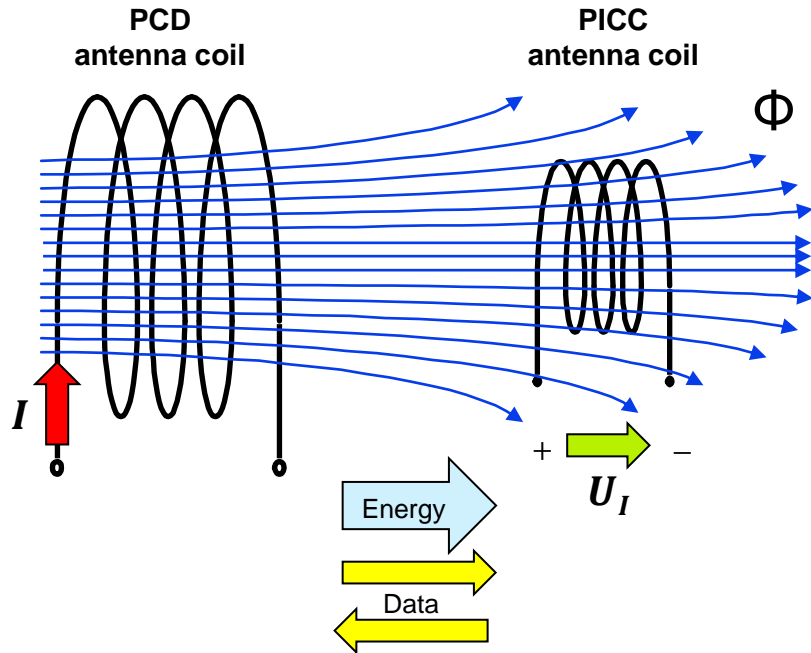

- ▶ The vast majority of RFID systems operate according to the principle of **inductive coupling**.
 - Typical contactless smartcards contain no internal power supply. They need to get all their required energy from the magnetic field in which they operate
- ▶ The PCD transmitter coil generates an electromagnetic field with a frequency of 13,56Mhz.
- ▶ A small part of the emitted field penetrates the antenna coil of the transponder, which is some distance away from the reader coil.
- ▶ A voltage U_I is generated in the transponder's antenna by inductance. This voltage is rectified and serves as the power supply.
 - A transformers-type coupling is created between the reader coil and the transponder coil.
- ▶ The PCD energy must be available to the PICC during the entire transaction.


NFC antenna: Transformer principle

Coupling coefficient

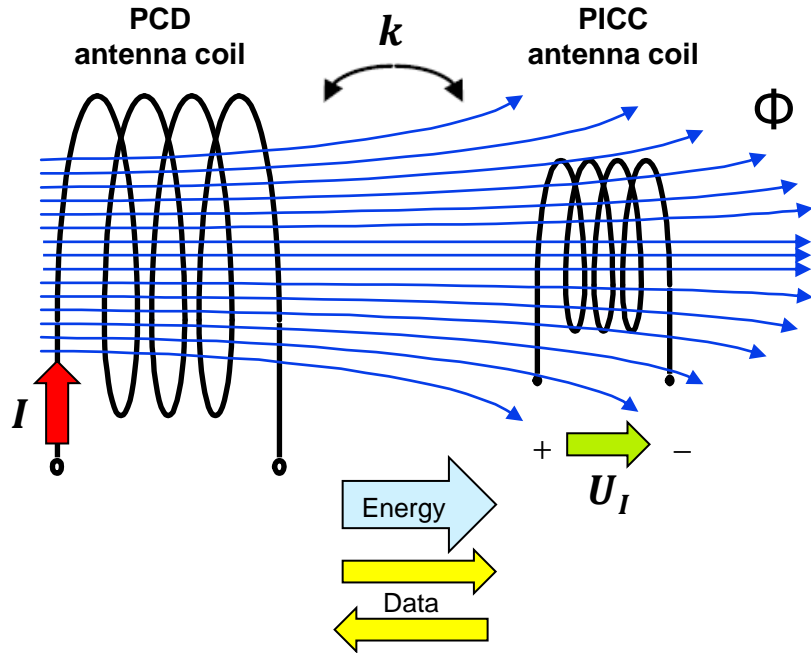

► The coupling coefficient depends on:

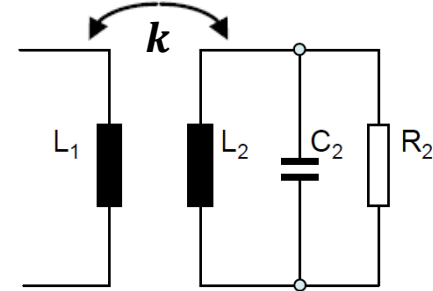- The geometric dimensions of both conductor loops.
- The position of the conductor loops in relation to each other
- The magnetic properties of the medium (μ_0)



$$0 < k < 1$$


$k = 1 \rightarrow$ total coupling

$k = 0 \rightarrow$ full decoupling


$$k = \underbrace{\mu_0}_{\text{Permeability constant}} \cdot \underbrace{\frac{r^2}{2\sqrt{(r^2+x^2)^3}}}_{\text{Geometrical quantity}} \cdot \underbrace{\frac{A_2}{\sqrt{L_{01} \cdot L_{02}}}}_{\text{"Fixed"}}$$

NFC antenna: Transformer principle

Mutual inductance

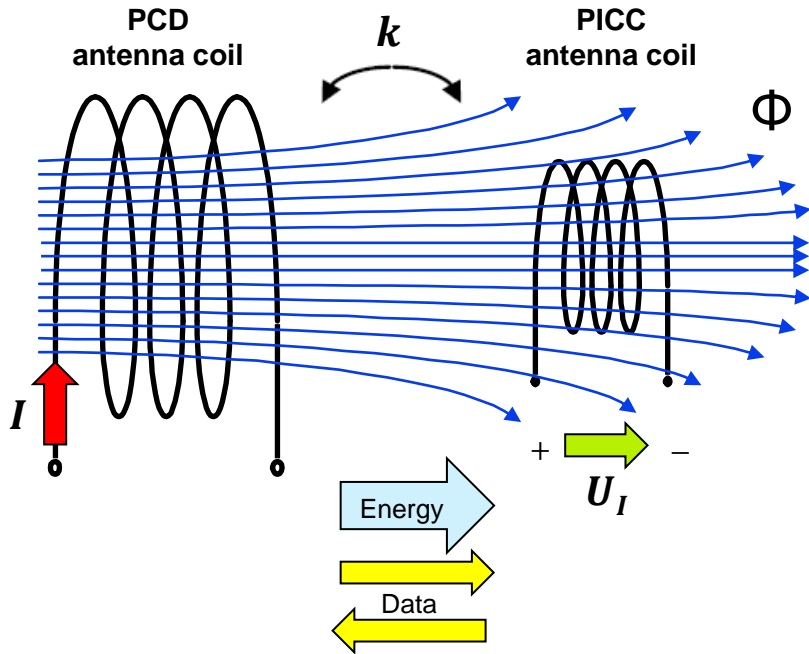

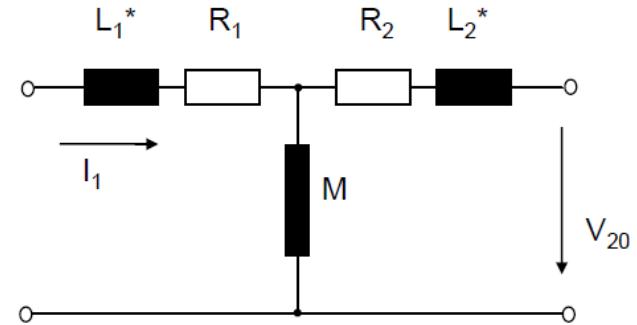
- The mutual inductance allows us to determine the voltage induced in the PICC antenna.
- This is a function of the coupling coefficient and the current provided in the reader antenna.



$$M = k \cdot \sqrt{L_1 \cdot L_2}$$

$$V_{20} = \omega \cdot M \cdot I_1$$

Optimum antenna size

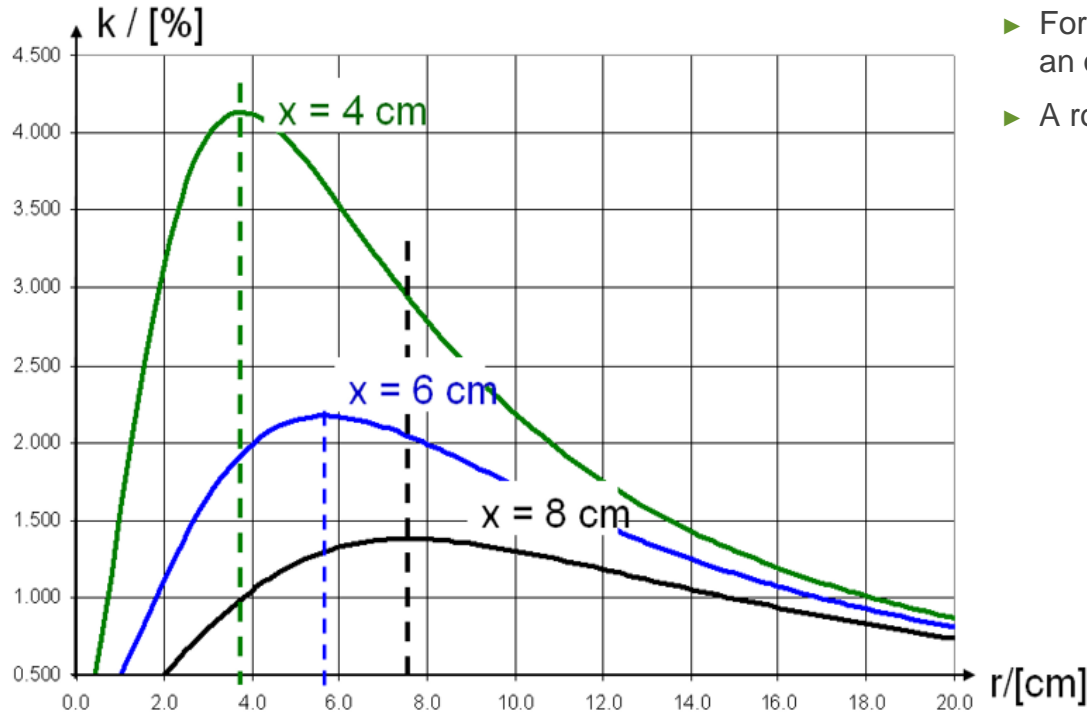


- For every read range x of an NFC system, there is an optimal antenna radius R .
- A rough approximation is that :

$$k = \mu_0 \cdot \frac{r^2}{2\sqrt{(r^2+x^2)^3}} \cdot \frac{A_2}{\sqrt{L_{01} \cdot L_{02}}}$$



$$r = x$$

Optimum antenna size

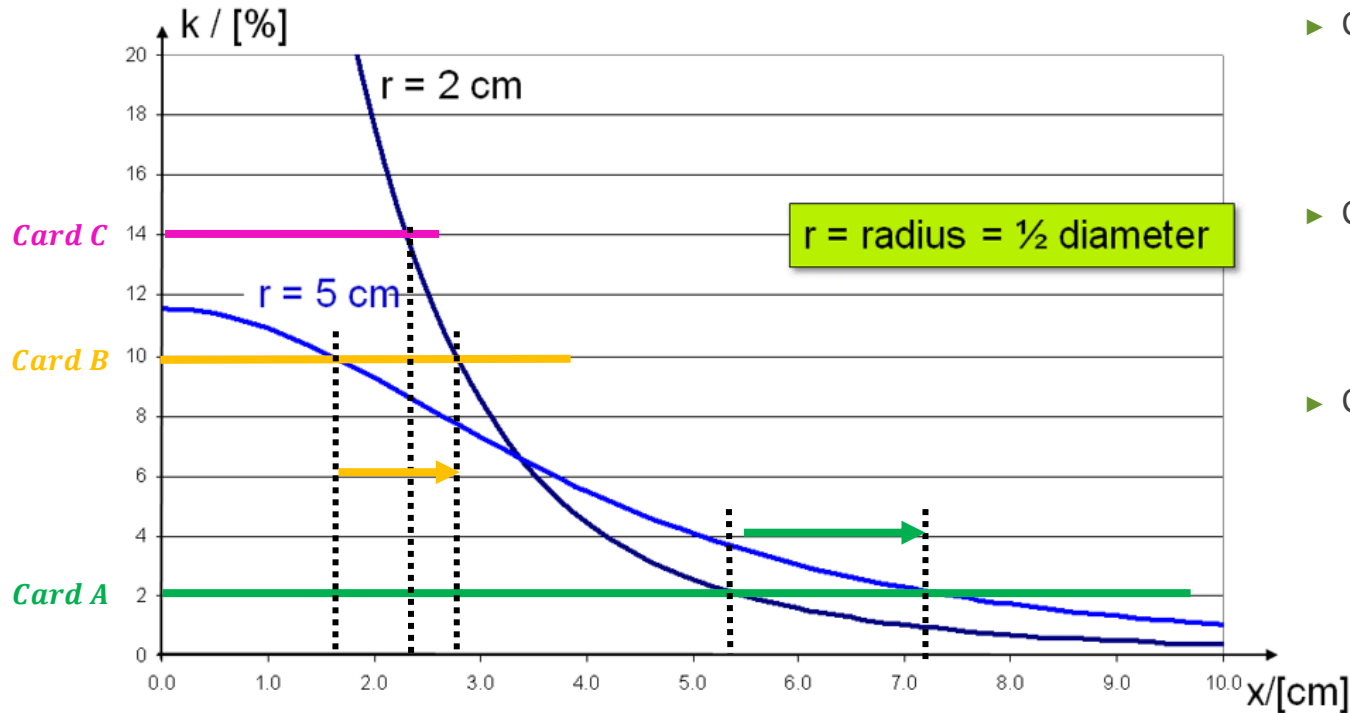

► Card A:

- PCD $r=2$ cm $\rightarrow x \approx 5.5$ cm
- **PCD $r=5$ cm $\rightarrow x \approx 7.2$ cm**

► Card B:

- **PCD $r=2$ cm $\rightarrow x \approx 2.2$ cm**
- PCD $r=5$ cm $\rightarrow x \approx -$ cm


► Card C:

- **PCD $r=2$ cm $\rightarrow x \approx 2.2$ cm**
- PCD $r=5$ cm $\rightarrow x \approx -$ cm

Antenna matching steps

NFC antenna matching steps

- 1** Define target impedance
To optimize RF output power or battery life
- 2** EMC filter design
Filtering of unwanted harmonics
- 3** Measure antenna coil
Determine LCR values of the antenna coil
- 4** Adjust Q-factor
With damping resistor if needed
- 5** Calculate matching components
Using provided excel sheet
- 6** Fine tuning
Simulation and field measurement
- 7** Adjust receiver circuit
Tuning reader sensitivity


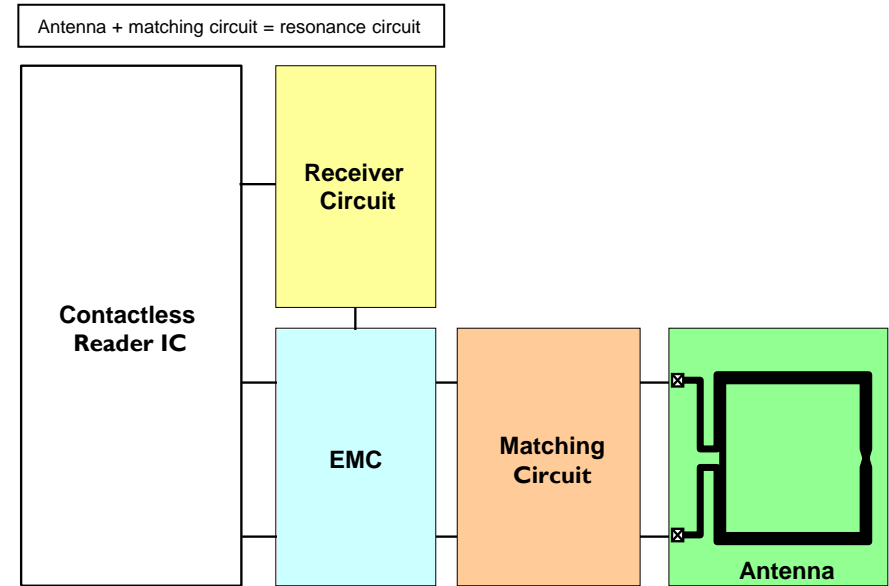


- ▶ [AN11019: CLRC663, MFRC630, MFRC631, SLRC610 Antenna design](#)
- ▶ [AN1445: Antenna design guide for MFRC52x, PN51x, PN53x](#)

NFC antenna matching

Step 1: Define target impedance

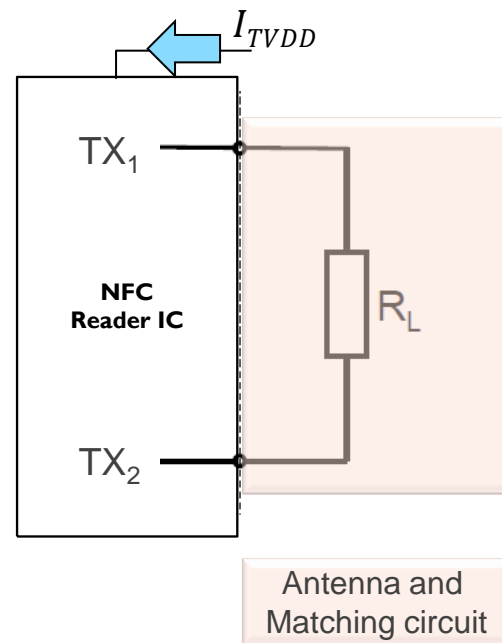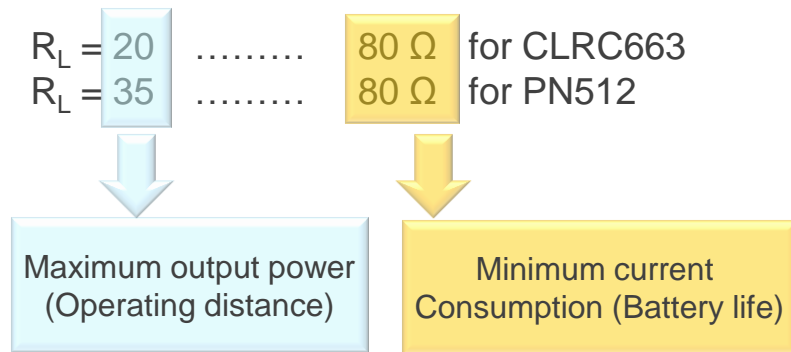
- ▶ We need to adjust the target impedance the NFC reader IC “sees” according to the performance we want to achieve.
 - Maximum output power
 - Minimum current consumption (battery life)
- ▶ The target impedance is chosen so that the highest possible output power does not exceed the maximum driver current (datasheet).



NFC antenna matching

Step 2: EMC filter design

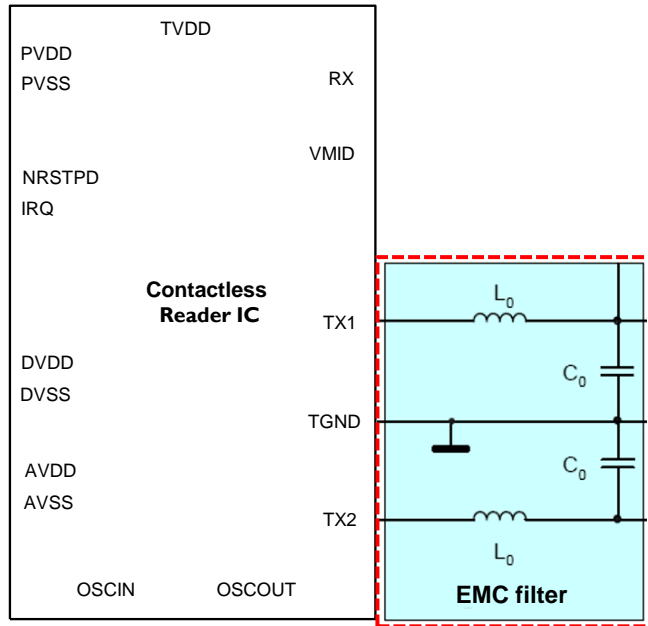- The EMC is a low pass filter reducing 2nd and higher harmonics and performs impedance transformation



- A convenient cutoff frequency (f_c) is between:

$$f_c = 14.5 \text{ MHz} \dots 22 \text{ MHz}$$

- We begin specifying L_0 , this range of values have proven to be very useful in practice:

$$L_0 = 330 \text{ nH} \dots 560 \text{ nH}$$

- With f_c and L_0 , we can easily calculate C_0 :


$$w_c = \frac{1}{\sqrt{C_0 \cdot L_0}} \Rightarrow C_0 = \frac{1}{(2 \cdot \pi \cdot f_c)^2 \cdot L_0}$$

- **Example:** $f_c = 21 \text{ MHz}$ and $L_0 = 470 \text{ nH}$:

$$C_0 = 122.2 \text{ pF} \Rightarrow \begin{aligned} C_{01} &= 68 \text{ pF} \\ C_{02} &= 56 \text{ pF} \end{aligned}$$

NFC antenna matching

Step 3: Measure antenna coil

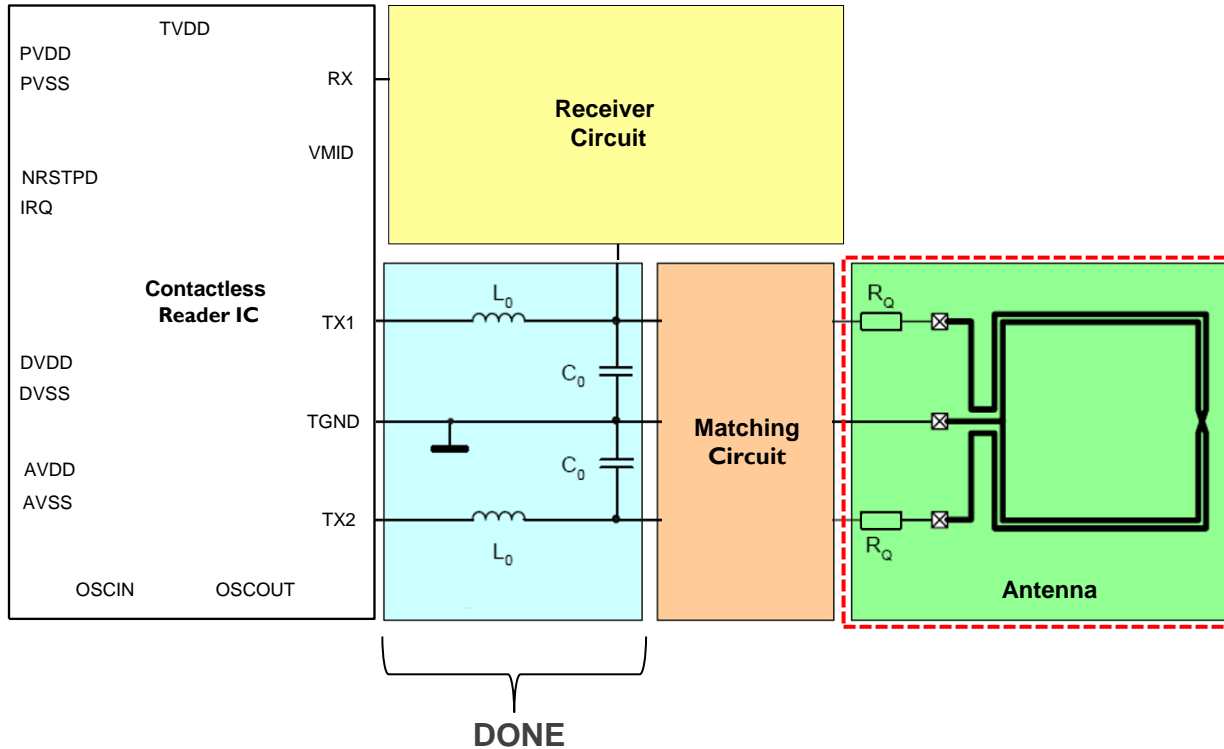

NFC antenna matching

Step 3: Measure antenna coil

- ▶ The antenna loop has to be connected to an impedance or network analyzer at 13.56 MHz to measure the series equivalent components

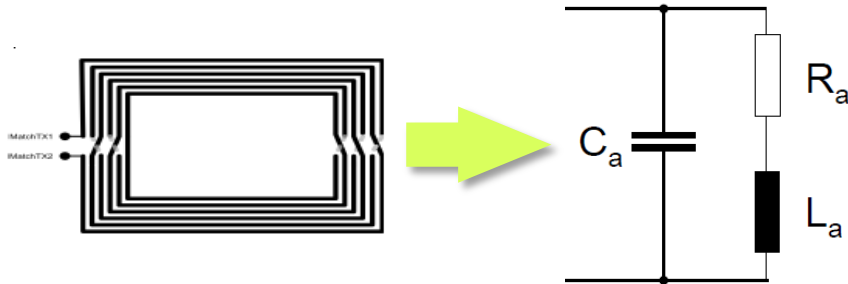


Fig. Antenna series equivalent circuit

Inductance (L): mainly defined by the number of turns of the antenna

Resistance (R): mainly defined by the diameter and length of the antenna wires

Capacitance (C): mainly defined by the distance of antenna wires from each other and number of turns

High-end network analyzer (i.e. Rohde & Schwarz ZVL)

- ▶ Powerful, accurate and easy to use



Low-end network analyzer (i.e. miniVNA PRO)

- ▶ Cheap, accurate enough and easy to use



NFC antenna matching

Step 3: Measure antenna coil

Practical approach:

- Measure L_a , R_a and estimate C_a
- And imprecise measurement suffices for us, as the measured values are needed only as starting points and the tuning will be done later.

$$L_a \approx 1.5 \mu H$$

$$R_a \approx 2.8 \Omega$$


$$C_a \approx ? \rightarrow C_a \approx 1 pF$$

- Typical values:

$$L_a = 0.3 \mu H \dots 4 \mu H$$

$$R_a = 0.3 \Omega \dots 8 \Omega$$

$$C_a = 1 pF \dots 30 pF$$

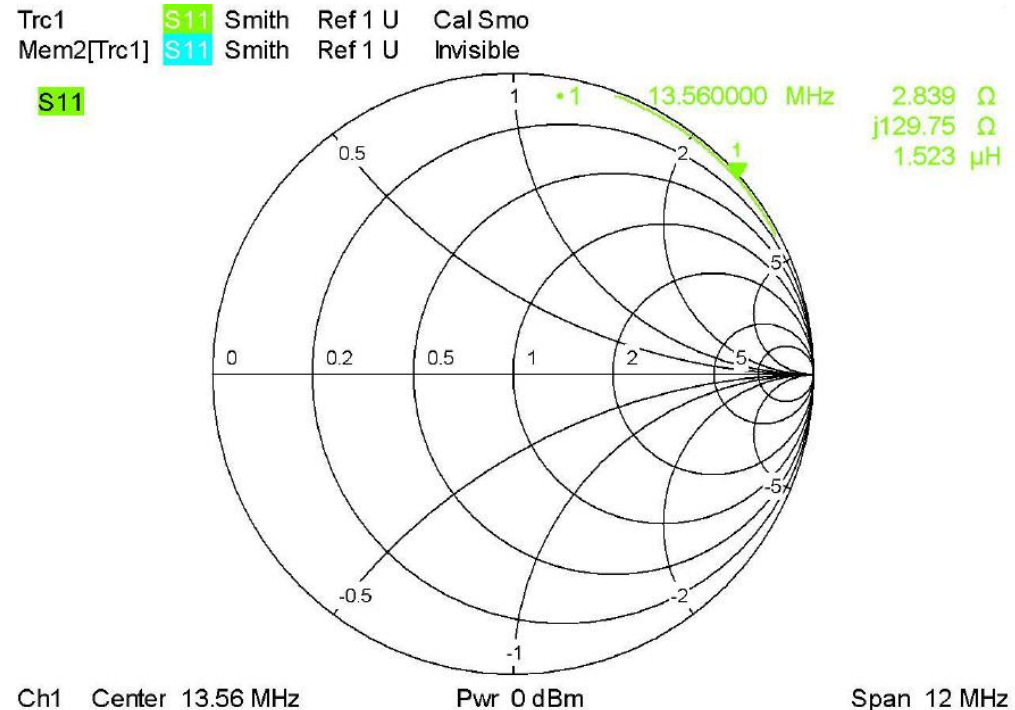


NFC antenna matching

Step 4: Adjust Q-factor

- ▶ A high Q factor leads to high current in the antenna coil and thus improves the power transmission to the transponder

$$B = \frac{f}{Q}$$

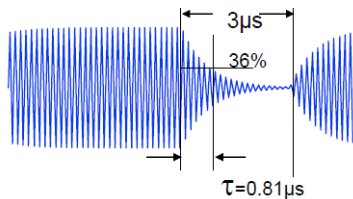- ▶ In contrast, the transmission bandwidth of the antenna is inversely proportional to the Q factor.
 - A low bandwidth, caused by an excessively high Q factor, can therefore significantly reduce the modulation sideband received from the transponder.



e.g.: ISO/IEC 14443-A @ 106Kbps

$$Q < f \cdot T$$

$$Q < 13.56\text{MHz} \cdot 3\mu\text{s}$$


$$Q < 40$$

- ▶ The quality factor of the antenna is calculated with:

$$Q_a = \frac{\omega \cdot La}{R_a}$$


- ▶ If the calculated Q_a is higher than the target value, an external damping resistor (R_q) has to be added.
- ▶ The value of (each side of the antenna) is calculated by:
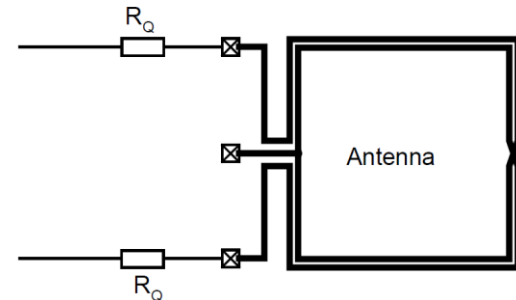
$$R_q = 0.5 \left(\frac{\omega \cdot La}{Q} \right)$$



NFC antenna matching

Step 5: Calculate matching components

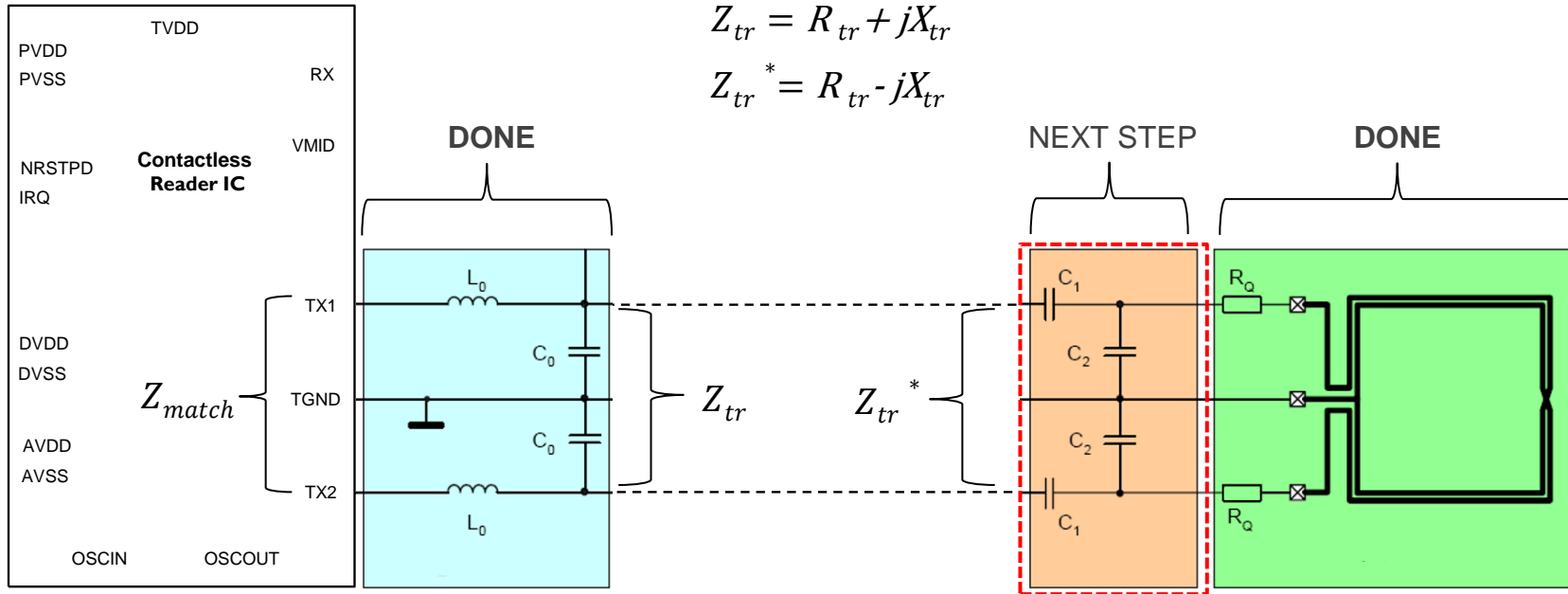

NFC antenna matching


Step 5: Calculate matching components (II)

- We input the following values into the excel sheet:

- Antenna coil measured / estimated values (L_a , C_a , R_a)
- Q-factor
- Target impedance (R_{match}).

- The excel sheet calculates the values for the matching circuit and damping resistor.

- R_Q , C_1 and C_2

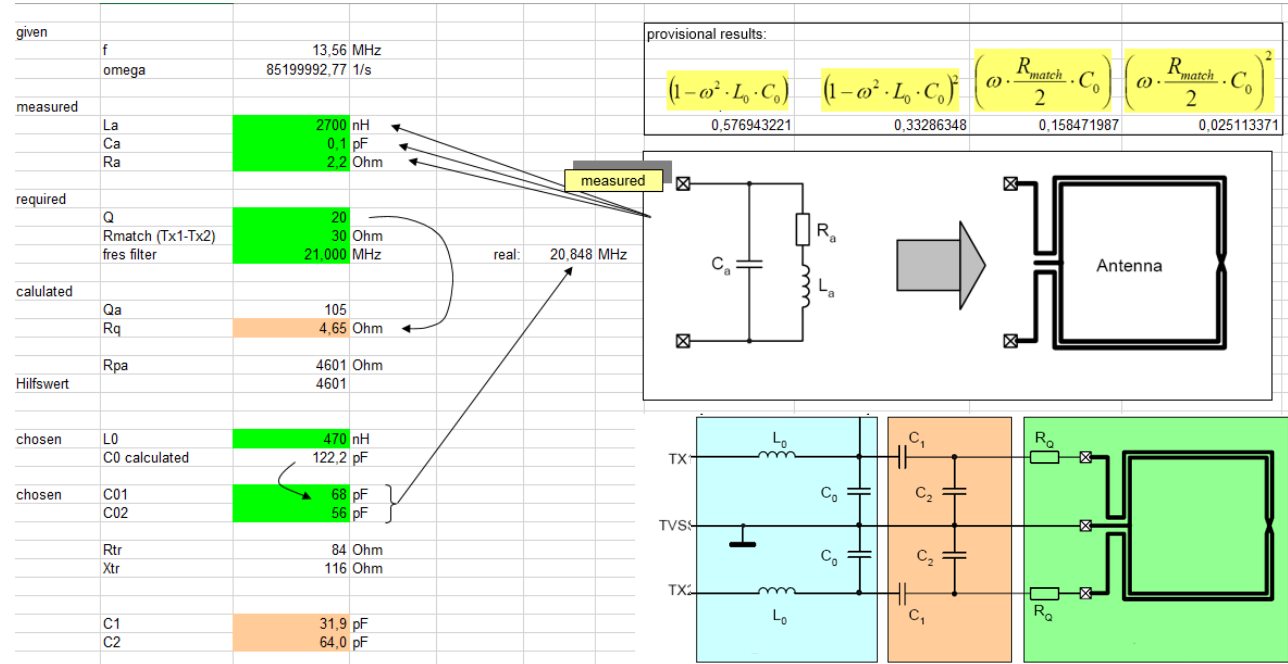


http://www.nxp.com/documents/other/AN11246_239810.zip

NFC antenna matching


Step 6: Fine tuning. Why is it required?

Simulation: RFSim99 software tool
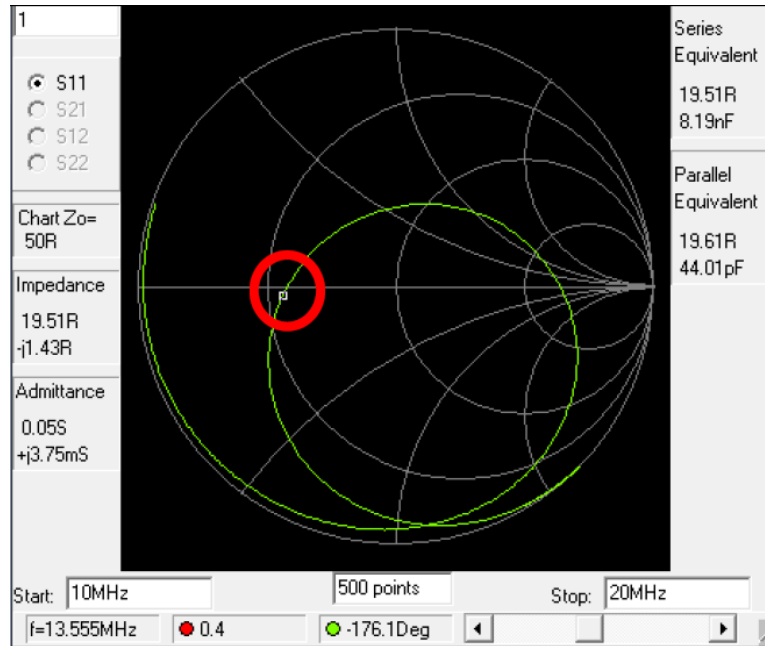
<http://www.electroschematics.com/835/rfsim99-download/>



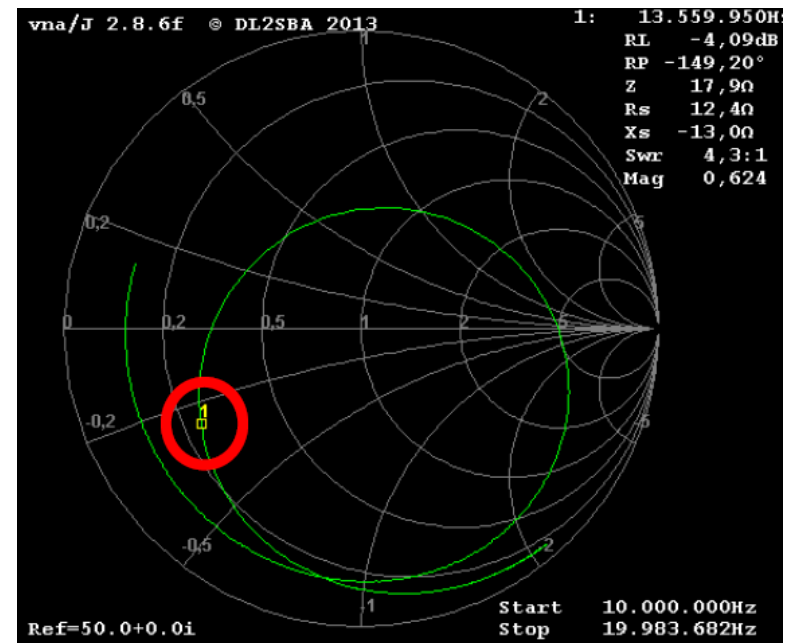
Reality: matching circuit assembled and measured with miniVNA




NFC antenna matching

Step 6: Fine tuning. Adapt simulation

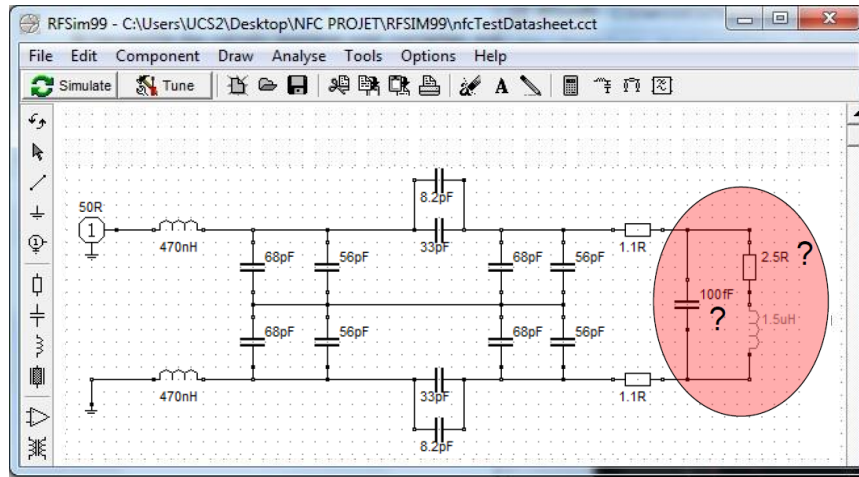
- ▶ Measured / estimated L_a , R_a and C_a antenna parameters are imprecise
- ▶ Tune R_a , C_a and L_a parameters until the simulation looks like the reality.



Reality
(miniVNA)

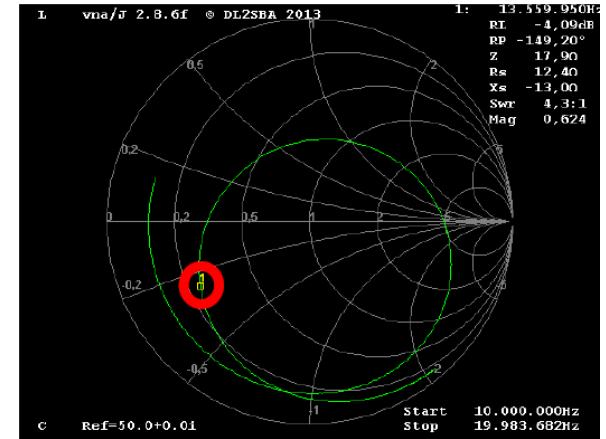


Simulation
(RFSim99)

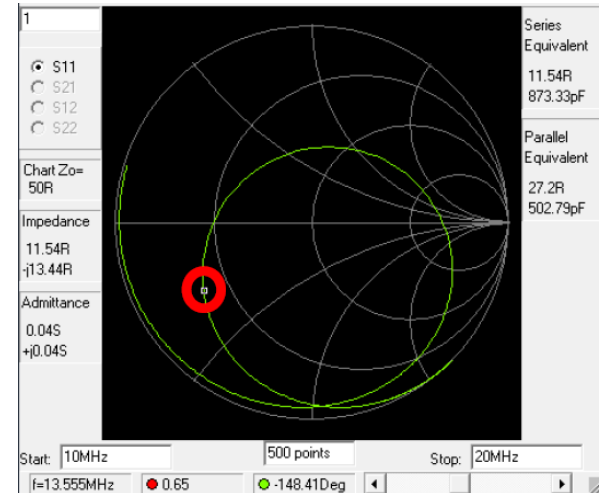



NFC antenna matching

Step 6: Fine tuning. Correct simulation

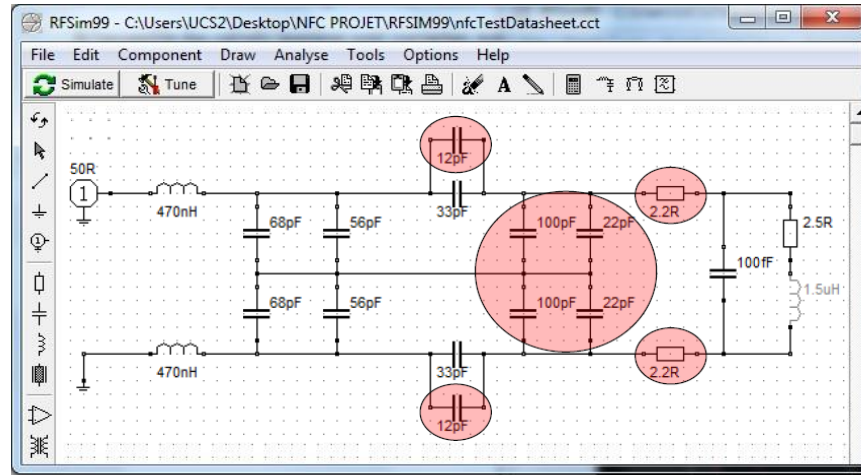


- ▶ Tune damping resistor (R_Q) and matching circuit capacitors (C_1 , C_2) until the simulated circuit is matched.
- ▶ Then, assemble the components again and measure reality.
- ▶ The actual adjustment may be reached through a process of iteration.

Simulation
(RFSim99)

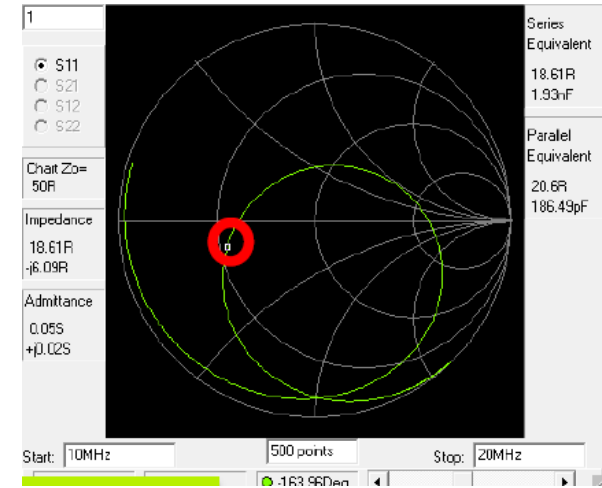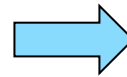


Reality
(miniVNA)

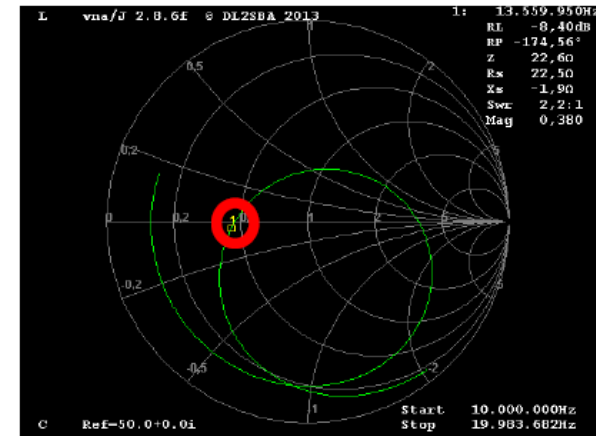

NFC antenna matching

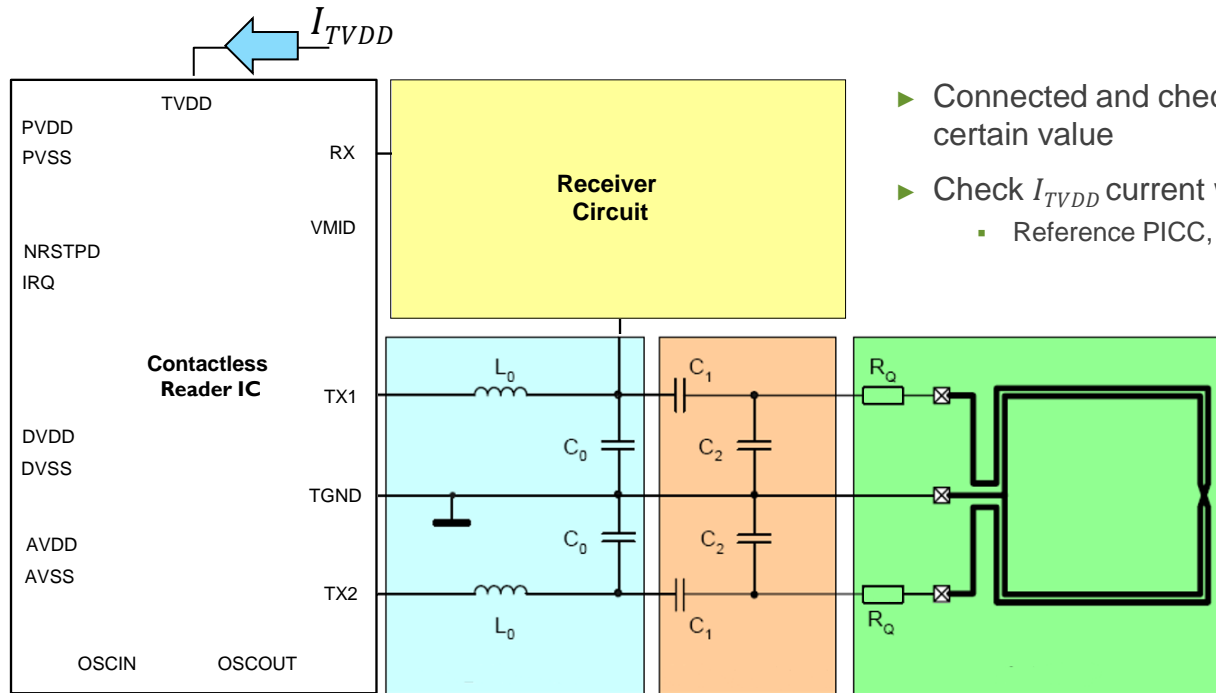Step 6: Fine tuning (II): Measurements on the Tx pulse



- ▶ Connected and check I_{TVDD} current does not exceed a certain value
- ▶ Check I_{TVDD} current without card and all loading conditions
 - Reference PICC, phone, different cards , etc

- ▶ For CLRC663 reader IC:


$$I_{TVDD} < 200 \text{ mA}$$

- ▶ For PN512 reader IC:

$$I_{TVDD} < 100 \text{ mA}$$


NFC antenna matching

Step 7: Receiver circuit

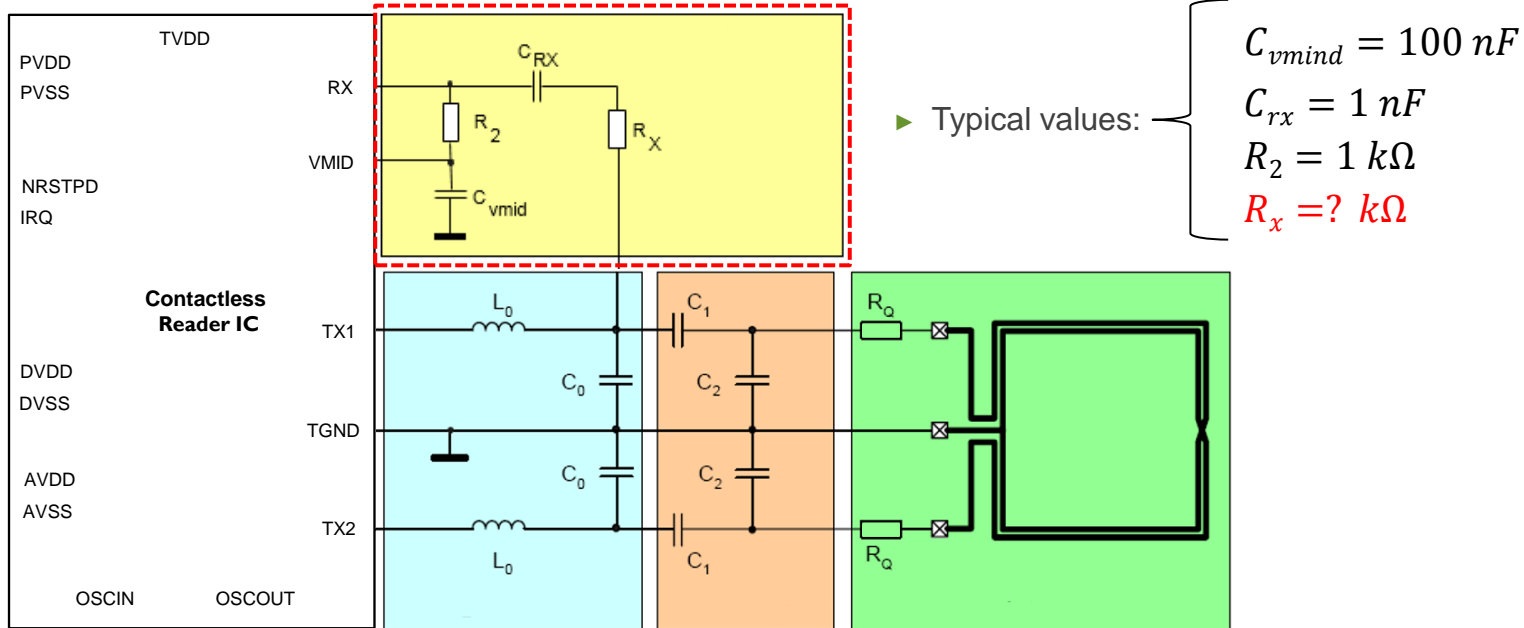

NFC antenna matching

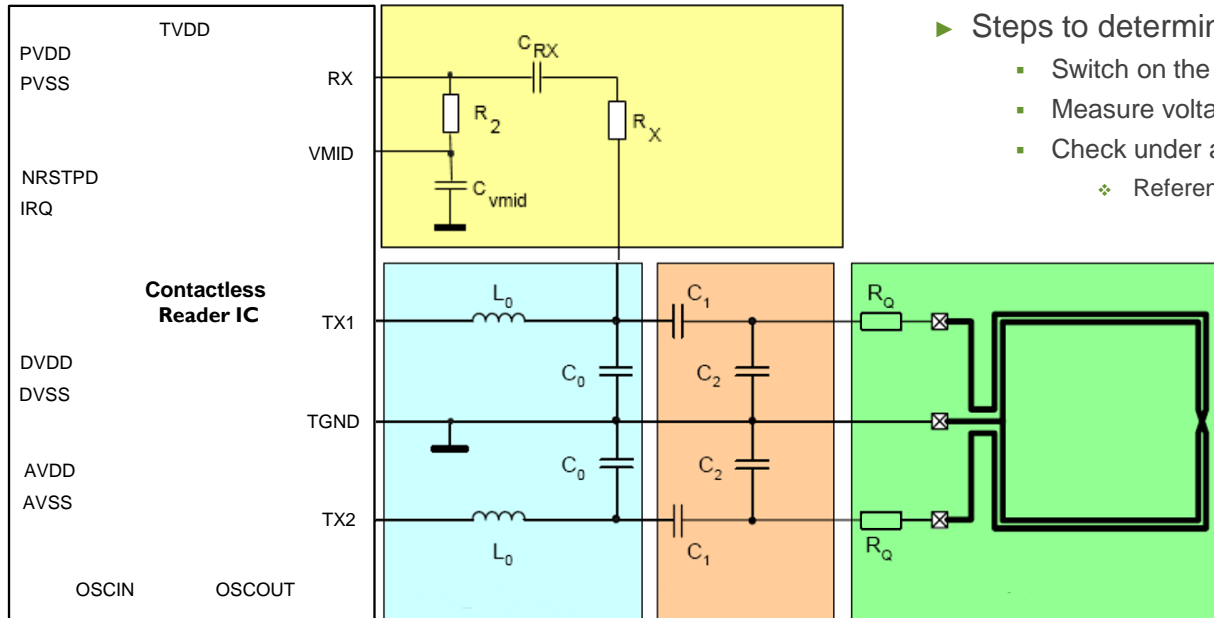Step 7: Receiver circuit. Adjust Rx level



► Steps to determine R_x :

- Switch on the Tx (continuous carrier)
- Measure voltage at R_x pin with a low capacitance probe (<2pF)
- Check under all loading conditions
 - ❖ Reference PICC, phone, different cards , etc

► For CLRC663 reader IC:

$$U_{Rx} < 1.7 V_{pp}$$



$$R_x = 12 k\Omega \dots 18 k\Omega$$


- If $U_{Rx} > 1.7 V_{pp} \rightarrow$ increase R_x
- If $U_{Rx} < 1 V_{pp} \rightarrow$ decrease R_x

Environment effects


Metal environment influences

Eddy currents

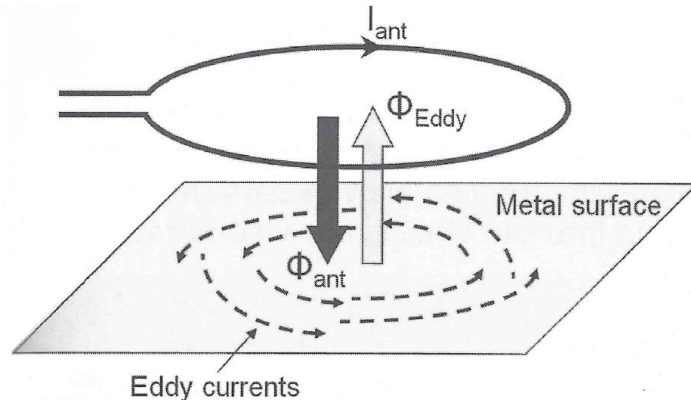- ▶ Metal surfaces in the immediate vicinity of the reader antenna have several negative effects.
- ▶ Our reader antenna's magnetic field generates eddy currents in metallic surfaces.
- ▶ These eddy currents produce a magnetic flow opposite to that of the reader device




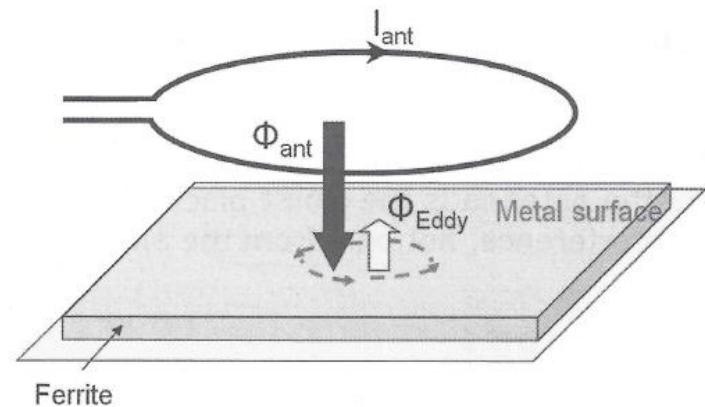- ▶ Ferrites are basically poor electrical conductors but are very good at propagating magnetic flux (mostly of iron oxide Fe_2O_3)
- ▶ The ferrite material “shields” the metal behind it.
- ▶ It significantly reduces the generated eddy currents






Shielding and environment impact

- ▶ The figures show three different field strength characteristics over reading distance x , for the same antenna coil:
 - Free air coil (7.5 cm)
 - Coil surrounded by a metal plate (5 cm)
 - Coil surrounded by a metal plate shielded by a ferrite plate (7.5 cm)
- ▶ We can achieve almost original operating distance using ferrite shielding. However, the ferrite detunes the antenna and produces:
 - Increase inductance
 - Increase Q-factor
 - Changed magnetic field distribution
- ▶ **Conclusion:** The antenna must be suited to its environment.

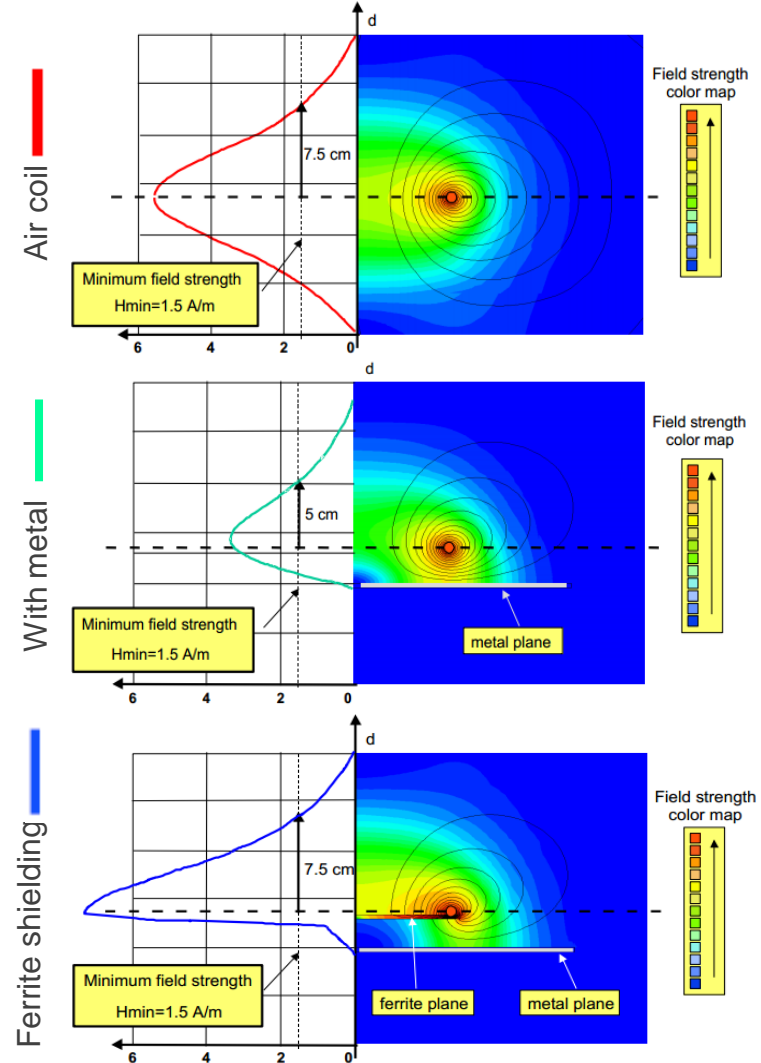


Ferrite shielding recommendation

- ▶ If the surface of the ferrite material is too small, the shielding effect will be too weak
- ▶ If it is too large, the field lines will become highly concentrated in the plane of the antenna and the ferrite.
- ▶ In practice, favorable dimensions have emerged for medium-sized antennas.
 - Where an overlap is created by having the ferrite material around 5mm larger than the antenna coil.
- ▶ Different ferrite foils have different effects, some foils:
 - Have a better Q.
 - Provide a better field distribution (reader mode).
 - Provide a better LMA (card mode)

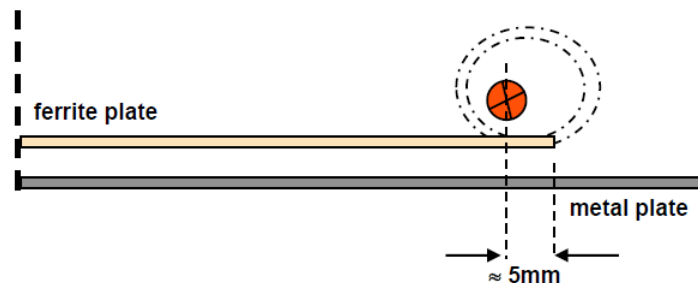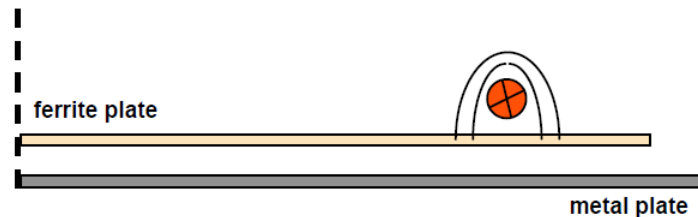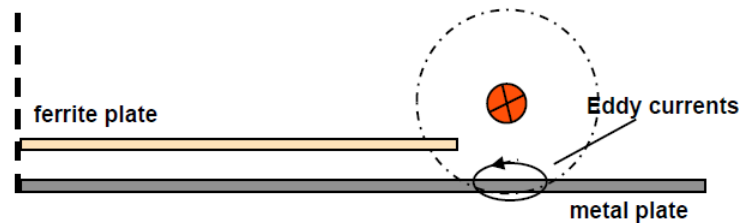

Test and Qualification

What must be tested?

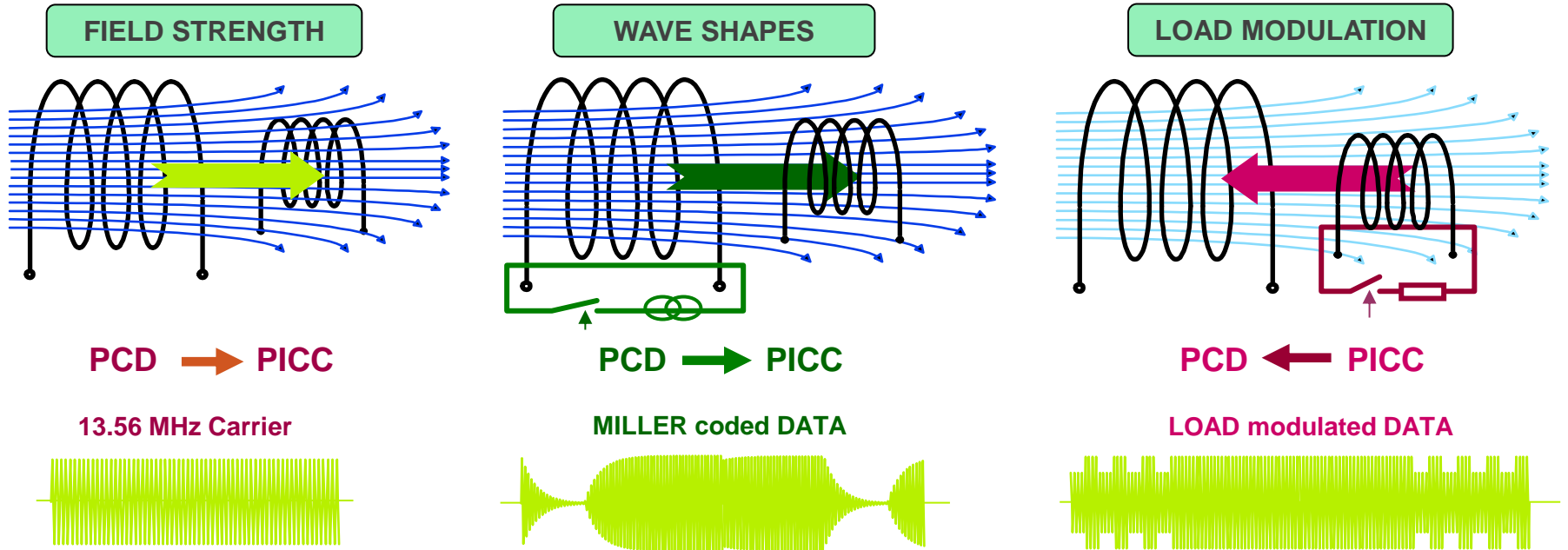

PCD: Proximity Coupling Device ("reader")
PICC: Proximity Integrated Circuit Card ("card")

Tests for NFC antenna performance

ISO/IEC 14443 tests:



- ▶ Test standard: **ISO/IEC 10373-6 Proximity cards**
- ▶ Tests for PICC and PCD
- ▶ Type A and Type B
- ▶ Bit rates: 106, 212, 424, 848 Kbps
- ▶ No certification available
- ▶ Applicable for public transport, access control, ePassport & eID etc

NFC Forum tests:



- ▶ Test standard: **NFC Analog Technical Specification**
- ▶ Mandatory for NFC Forum devices
- ▶ NFC-A, NFC-B & NFC-F
- ▶ Defines analog tests for NFC devices (P2P, Reader and Card modes)
- ▶ Bit rates: 106, 212, 424 Kbps
- ▶ Certification process available for NFC compliance
- ▶ Applicable for mobile phones

EMVCo tests:



- ▶ Test standard: **EMV Contactless Specifications for Payment Systems (Book D)**.
- ▶ Test for PICC and PCD
- ▶ Type A and Type B
- ▶ Only for 106 Kbps


ISO/IEC 14443 Field strength test

Field strength test condition:

- ▶ Measure reader maximum reading distance.
 - Minimum field strength defined by ISO/IEC 14443 is 1.5 A/m

Tools: Reference PICC

- ▶ Reference PICC are designed specifically to allow complete conformance testing of contactless readers according to ISO/IEC 10373
- ▶ Pick up coil:
 - Allows to measure the PCD pulse shapes.
 - Low coupling between the two coils.
- ▶ Main coil:
 - Represents the “real smartcard”.
 - Loads the field like a read card and allows to measure field strength and test load modulation
- ▶ ISO/IEC 10373-6 defines 6 reference PICCs :

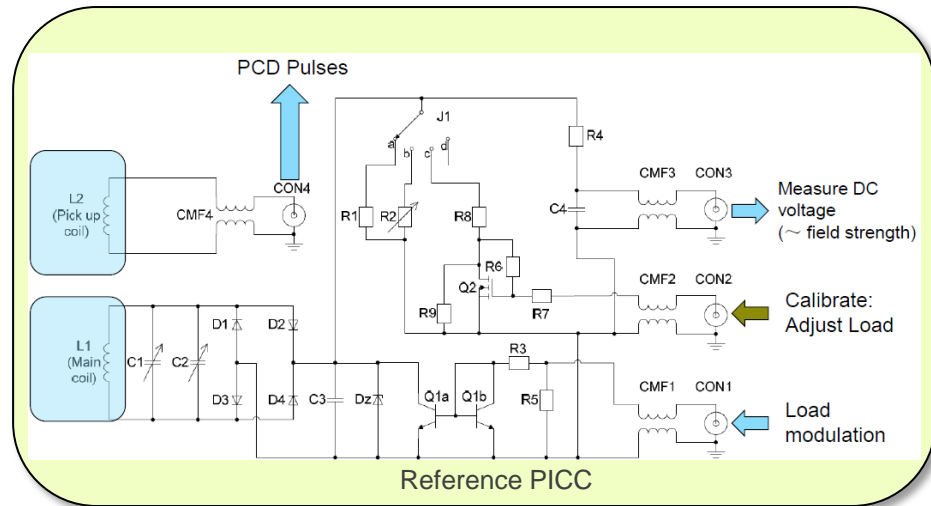

ISO/IEC 14443 Wave shapes test



Type A @106kbps

Wave shape test condition:

- ▶ Measure pulse shape in maximum reading distance
 - This is of course the worse possible case
- ▶ Requirements for the wave shapes are fixed in the ISO/IEC14443 standard for the different data rates
 - Pulse length, rise and fall times, overshoots etc

Tools: Wave checker tool

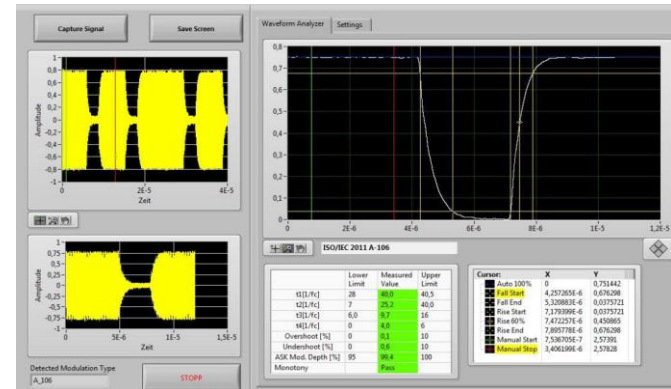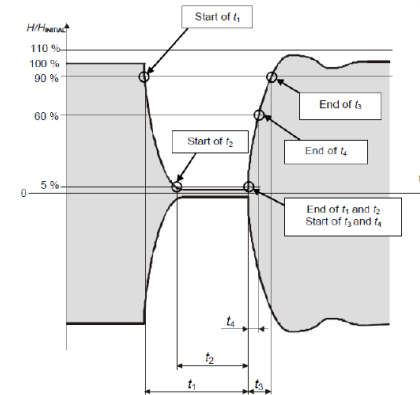- ▶ PC tool that takes shoot from the scope, reads the data, checks the pulse shapes and compares it within the ISO/IEC limits.
- ▶ E.g.: Wavechecker from CETECOM
 - Flexible tool supporting measurements for ISO/IEC, NFC Forum or EMVCo.




ISO/IEC 14443 Load modulation test

Load modulation test condition:

- ▶ Check if our reader can decode card responses properly in the maximum reading distance
- ▶ Inject a certain level of load modulation using a sub carrier pattern

Tools: Arbitrary Wave Generator (AWG) & PC Tools

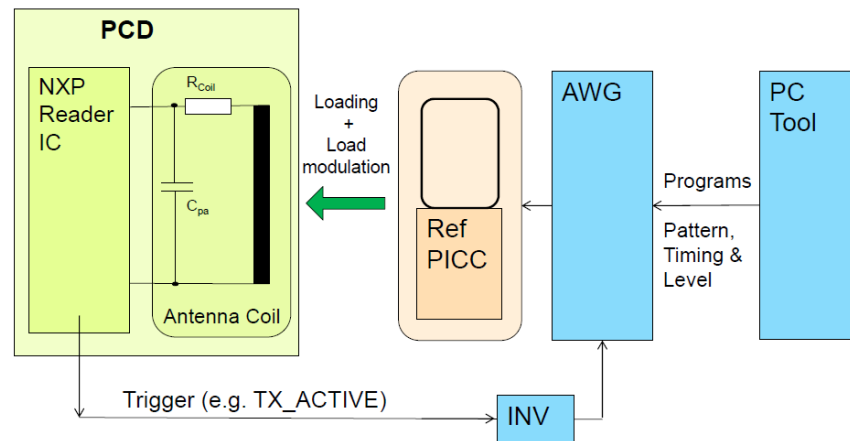- ▶ Creates or generates pattern subcarriers together with a PC tool that allow us to define patterns and timing levels.
- ▶ E.g: Waveplayer from CETECOM as AWG
 - Includes many predefined patterns and flexible tests (ISO/IEC 14443-A & B, EMVCo)
 - Control level and timing of the load modulation index – amplitude signal.




NFC Forum and EMVCo tests

“Reference PICCs”


► NFC Forum major analog NFC reader parameters:

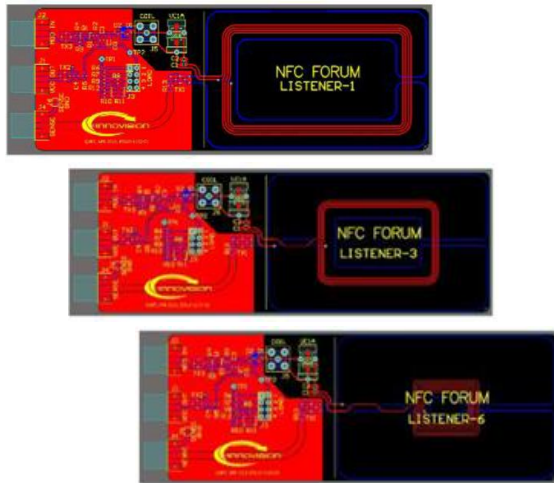- Polling Device Power Transfer (“Field strength”)
- Polling Device Modulation (“Wave shapes”)
- Polling Device Load Modulation (“Load Modulation”)
- Many more Listening Device parameters: not part of this webinar.



► EMVCo major analog PCD parameters:

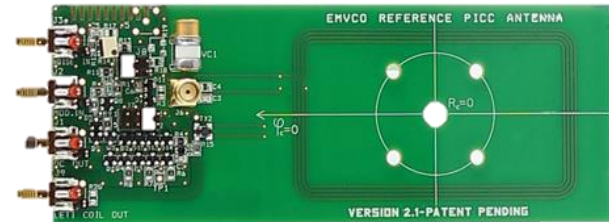- Power Transfer PCD to PICC (“Field strength”)
- Requirements for Modulation PCD to PICC (“Wave shapes”)
- Requirements for Modulation PICC to PCD (“Load modulation”)



NFC antenna design

Wrap up

- ▶ NFC antennas are “transformers in resonance”
- ▶ The size (geometry) of an RFID/NFC antenna defines the operating distance (“performance”) in principle:
 - Small size = small operating distance
 - Large size = large operating distance
- ▶ Metal around or behind the NFC antenna “kills” the magnetic field. Can be shielded with ferrite.
- ▶ The final design of an RFID/NFC antenna is quite straight forward with the right tools.
- ▶ Different requirements depending on ISO/IEC1443, NFC Forum and EMVCo
 - Use the correct reference tools (ref PICCs, Oscilloscope, PC tools
 - Or use test house services

Further information

NFC Reader Design: Antenna design considerations

- ▶ NFC Everywhere community
<http://www.nxp.com/techzones/nfc-zone/community.html>
- ▶ NFC controller and frontend solutions
http://www.nxp.com/products/identification_and_security/nfc_and_reader_ics/
- ▶ RFID: MIFARE and Contactless Cards in Application (**Co-author: Renke Bienert**)
www.amazon.com/RFID-MIFARE-Contactless-Cards-Application/dp/1907920145
- ▶ In-depth NFC antenna design recorded webinars (**Renke Bienert**):
 - **Antenna design webinar 1:** Which antenna for what purpose?
 - **Antenna design webinar 2:** Antenna matching
 - **Antenna design webinar 3:** Metal environment
 - **Antenna design webinar 4:** Optimization and debugging
 - **Antenna design webinar 5:** Test & Qualification
 - **Antenna design webinar 6:** EMC related design

MobileKnowledge

Thank you for your attention

- ▶ We are a global competence team of hardware and software technical experts in all areas related to contactless technologies and applications.
- ▶ Our services include:
 - Application and system Design Engineering support
 - Project Management
 - Technological Consulting
 - Advanced Technical Training services
- ▶ We address all the exploding identification technologies that include NFC, secure micro-controllers for smart cards and mobile applications, reader ICs, smart tags and labels, MIFARE family and authentication devices.



For more information

Eric Leroux
eric.leroux@themobileknowledge.com
+34 629 54 45 52